

ENEE2360 Project2



The room thermostat circuit shown in Fig.(1) is used to maintain the room temperature within predetermined temperatures $T(\text{max})$ and $T(\text{min})$

Part1(Practical)

- a) Construct the circuit to verify its function.
- b) By changing the 47k pot, determine the value of V_x so that $V_{o2} = +V_{sat}$ and the LED is off at room temperature.
- c) By changing the 47k pot, determine the value of V_x so that $V_{o2} = -V_{sat}$ and the LED is on at room temperature.

Part2 (Simulation and reporting)

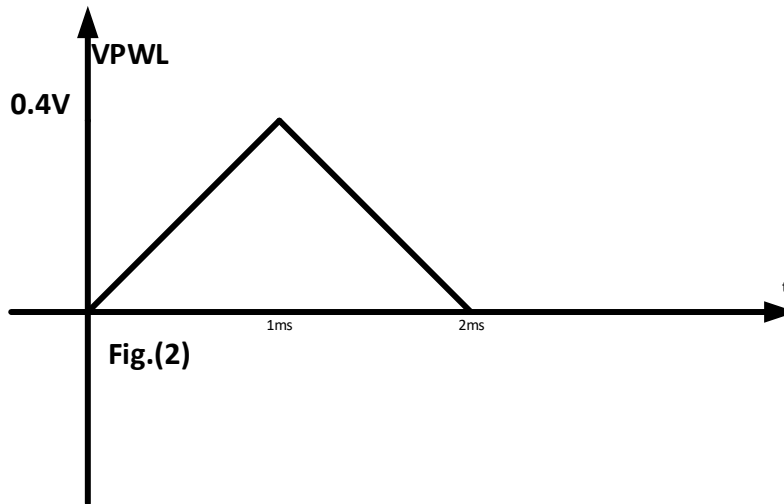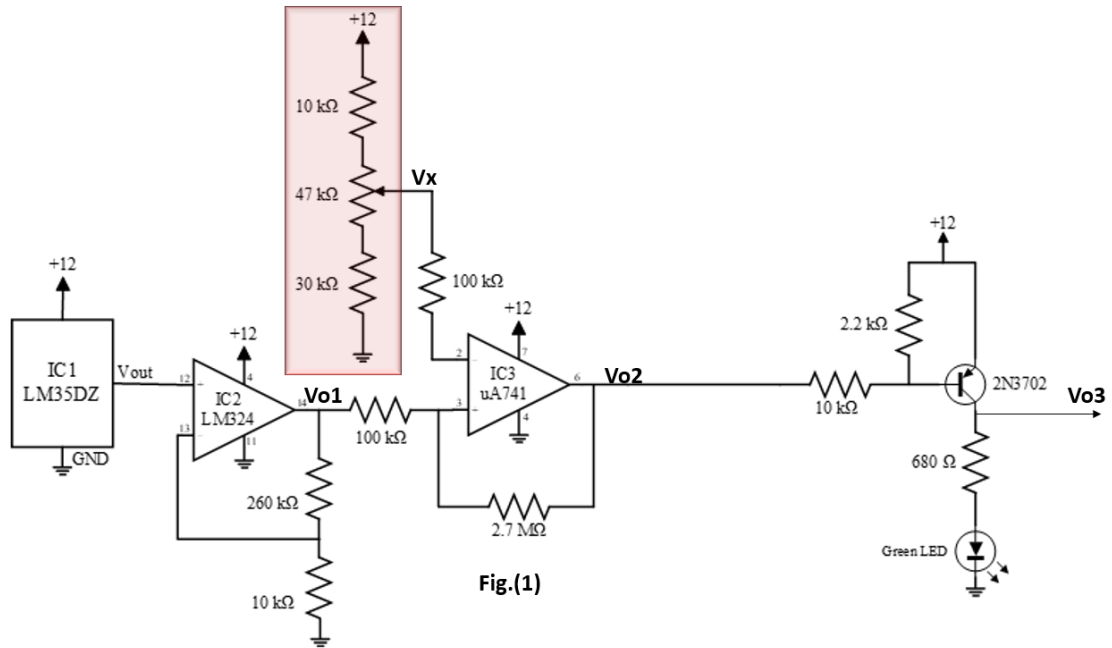- a) Replace the circuit to the left of V_x by a 6V battery.
- b) Replace the green LED with D1N4002
- b) Replacing the temperature sensor by a VPWL Voltage source as shown in Fig.(2) , plot V_{o1} , $V_{o2}(t)$, and $V_{o3}(t)$.
- c) Estimate the upper threshold and the lower threshold temperatures from V_{o1} and $V_{o2}(t)$ plots.
- d) Determine $+V_{sat}$ and $-V_{sat}$
- e) Using results of part d, calculate by hand the upper threshold and the lower threshold temperature.
- f) Write a simple report which includes:
 - 1 – Explanation of the function of the circuit of Fig.(1)
 - 2 - Simulation circuits and results
 - 3 - Comparison of simulation results to hand calculation
 - 4 – Conclusion



GOOD LUCK